

## Unleashing the LM386

Sverre Holm, LA3ZA,  
<http://www.qsl.net/la3za/>  
Dæliveien 1, NO 1383 Asker, Norway.

The LM386 must be one of the most popular audio output amplifiers among radio amateurs, despite having been around for a long time. It can be obtained in both dual-in-line and surface-mount packages and outputs 325 mW in the standard version that runs from 4-12 Volts supply voltage. Its voltage gain of 46 dB is in many cases too little, especially in direct conversion receivers. When I built the Pixie 2 with the LM386 audio stage, it struck me how the sensitivity of the receiver was limited by the audio gain. I asked myself if it would be possible to increase the gain and add some filtering without in a simple way, and the result is a gain of more than 70 dB and an audio bandwidth of a few hundred Hz by only adding 3 resistors, 1 capacitor and an inductor.

### Analysis of the LM386 Amplifier

The basic LM386 amplifier is used without any feedback between pins 1, 5, and 8. The standard way for getting a larger gain is to connect a large capacitor (say 10  $\mu$ F) between pins 1 and 8. In either case, the voltage gain equation is:

$$A_{v,1} = \frac{2Z_{1-5}}{150 + Z_{1-8}}$$

Here  $Z_{1-5}$  and  $Z_{1-8}$  are the impedances between the respective pins. This equation describes the feedback path from the output to the emitter of the input stage, where the factor 2 is due to the differential input stage.  $Z_{1-5}$  must also include the built-in 15k resistor which is in parallel to external circuitry, and likewise  $Z_{1-8}$  should include the built-in 1.35k resistor. Thus, without external components, it has a gain of  $A_v = 2 \cdot 15k / (150 + 1350) = 20$  or 26 dB and with a large capacitor between pins 1 and 8 it has a gain of  $A_v = 2 \cdot 15k / 150 = 200$  or 46 dB.

The application note of the LM386 suggests a bass boost by connecting 10k in series with 33nF between pins 1 and 5 with pin 8 open, while a common set of values among radio amateurs is in the order of 2.2k and 4.7nF. The effect is a roll-off at frequencies above 1-2 kHz. The effect can be analysed with the gain equation above by inserting  $2.2e3 + 1/(j2\pi f 4.7e-9)$  in parallel to the 15k internal feedback resistor. I use Matlab for this kind of analysis.

### Additional Gain

The LM386 data sheet says "Gain control can also be achieved by capacitively coupling a resistor from pin 1 to ground." The effect of a low value resistor here is to decrease feedback and increase gain. JF1OZL has measured the gain with various resistors and by going as low as to a 3.3 ohms resistor, he got 74 dB, see <http://www.intio.or.jp/jf1Ozl/LM386.htm>. In this case, the feedback consists of a division between the  $Z_{1-5}$  and the  $Z_{1-gnd}$  impedances, indicating that the gain is found from the equation of an inverting feedback amplifier:

$$A_{v,2} = \frac{A_0}{1 + A_0 \frac{Z_{1-gnd}}{Z_{1-5}}} \approx \frac{Z_{1-5}}{Z_{1-gnd}}$$

The approximation is in the case that the open-loop gain,  $A_0$ , is much larger than the closed-loop gain,  $A_{v,2}$ . This will give a gain of  $15000/3.3 = 4546 = 73.2$  dB which is close enough to JF1OZL's

measurement. Such a high gain requires careful circuit layout with attention to ground loops and proper decoupling, or the amplifier will oscillate. I have measured a gain of over 80 dB in a well-decoupled circuit, but then the amplifier is at the verge of self-oscillation.

## High Gain and Filtering

The two ideas above can be combined in order to get both a high gain and high frequency roll-off. Further, if the circuit between pin 1 and ground is a series resonance circuit, the bandpass characteristic can be made even sharper. An inductor of 1 mH will resonate with the 100  $\mu$ F capacitor at about 500 Hz and is fine. The problem now is that the gain will drop so much at the higher frequencies that it gets below the value of 9 which is the stability limit for the LM386. To limit the attenuation at high frequencies, the inductor has to be paralleled with a resistor and a value of 220 ohms or less seems to be adequate. A potentiometer in series with the inductor makes the gain variable. The resulting schematic is shown in Fig. 1.


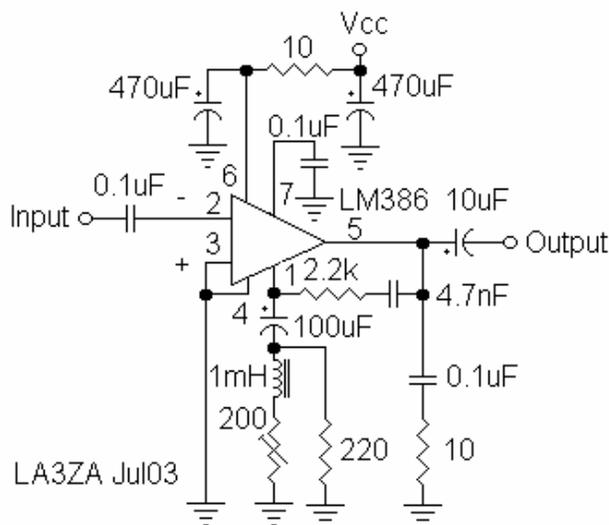


Figure 1. LM386 with enhanced gain and filtering

## Measurements

Measurements were made for this circuit with an LM386-N1 with date code 99 from National Semiconductors at a supply voltage of 9 Volts, no output load, and no input coupling capacitor. In this circuit, the DC resistance of the 1 mH inductor of about 2 ohms, and the equivalent series resistance of about 0.5 ohms of the 100  $\mu$ F capacitor play a role and must be accounted for. The upper curve is with no series resistance except for those of the inductor and capacitor, the middle curve is with a total resistance of 10 ohms, i.e.  $10 - 2 - 0.5 = 7.5$  ohms series resistance, and the lower one is for the pot at its maximum value of 200 ohms.

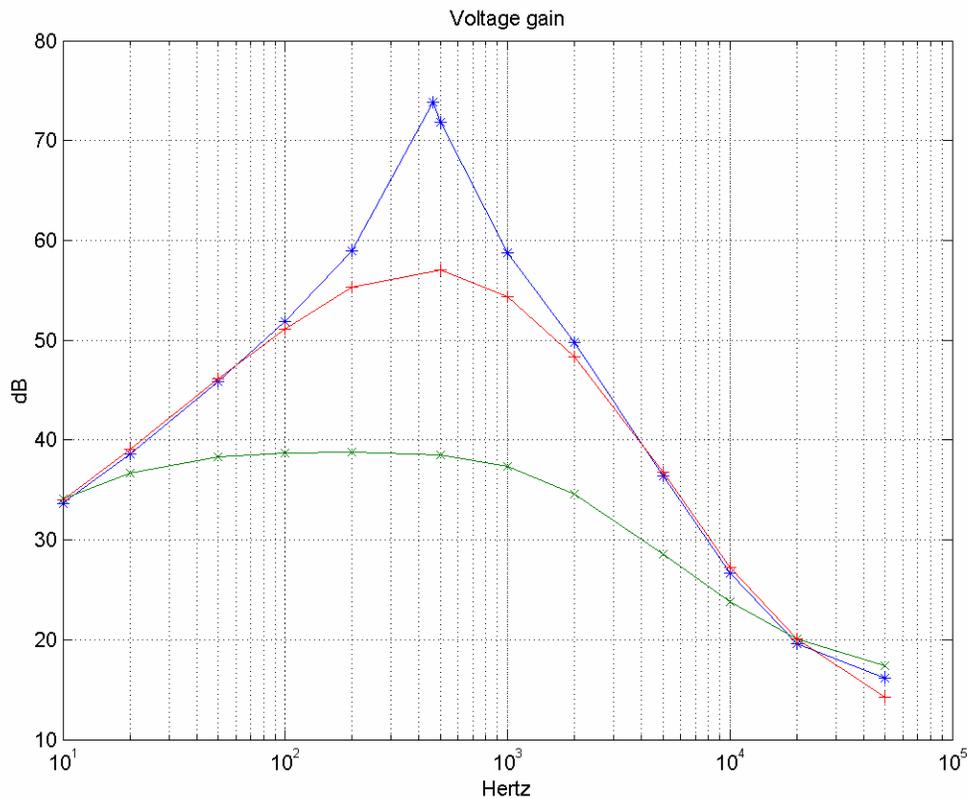

**Figure 2. Measurements with R = 2.5, 10, and 200 ohms**

## Discussion

I tried different LM386-N1's in this circuit and found that the peak gain of the highest curve would vary. Another chip with date code 99 gave 2 dB more gain, while a third one with date code 92 had 7 dB lower gain. I also tried a surface mount LM386-M1 dated 93 which had 5 dB less gain. In all cases, the gain at 1 kHz hardly changed at all. Also, the peak gain is sensitive to output load. The peak value of the highest curve would fall by 8 dB with a 32 ohm load, while hardly changing at all at 1 kHz. These results suggest that the gain,  $A_{v,2}$  depends on the open-loop gain, and that the open-loop gain varies from batch to batch.

The muting of the amplifier by means of pin 7 (SPRAT no. 113, Winter 2002/3, pp18-20), is still possible, but only if pin 7 is connected to Vcc. Grounding of pin 7 will only mute the amplifier in the basic 26 and 46 dB circuits, while the amplifier of Fig. 1 will instead output a low-level low frequency noise.

I also tried to find the gain equation for the circuit in Fig. 1 and my guess was  $A_v = A_{v,1} + A_{v,2}$ . However, this equation overestimates gain by something like 8 dB except for the peak of the highest curve. Maybe some readers who are more into the inner workings of this amplifier can come up with a better equation.

In summary, addition of a few components to the basic LM386 amplifier results in a response which is fine for CW reception with a peak in the 500 Hz range. The amplifier also has enough gain for a direct conversion receiver with a passive mixer like the Pixie 2, that it in many cases it can drive a loudspeaker. Hopefully, the circuit can benefit other direct conversion receivers also.